


The Three States of Operation

- **Active or Linear Region Operation**
Base-Emitter junction is forward biased
Base-Collector junction is reverse biased
- **Cutoff Region Operation**
Base-Emitter junction is reverse biased
Base-Collector junction is reverse biased
- **Saturation Region Operation**
Base-Emitter junction is forward biased
Base-Collector junction is forward biased

DC Biasing Circuits

- Fixed-bias circuit ✓
- Emitter-stabilized bias circuit
- Voltage divider bias circuit ✓
- DC bias with voltage feedback

1. Fixed Bias

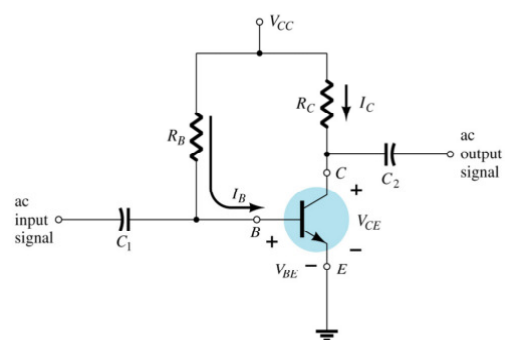


The Base-Emitter Loop

From Kirchhoff's voltage law:

$$+V_{CC} - I_B R_B - V_{BE} = 0$$

Solving for base current:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

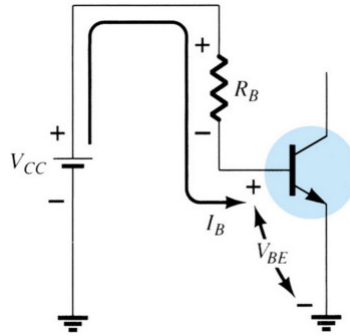

Collector-Emitter Loop

Collector current:

$$I_C = \beta I_B$$

From Kirchhoff's voltage law:


$$V_{CE} = V_{CC} - I_C R_C$$

Saturation

When the transistor is operating in saturation, current through the transistor is at its *maximum* possible value.

$$I_{C\text{sat}} = \frac{V_{CC}}{R_C}$$

$$V_{CE} \cong 0 \text{ V}$$

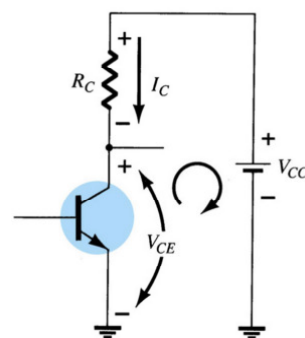

Load Line Analysis

The end points of the load line are:

I_{Csat}


$$I_C = V_{CC} / R_C$$

$$V_{CE} = 0 \text{ V}$$

$V_{CEcutoff}$

$$V_{CE} = V_{CC}$$

$$I_C = 0 \text{ mA}$$

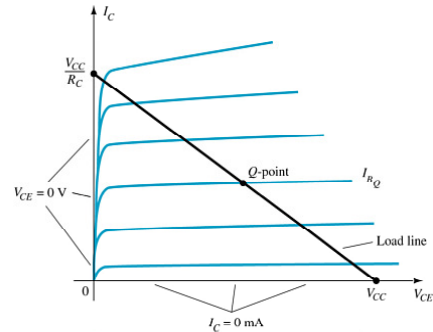


The Q -point is the operating point:

- where the value of R_B sets the value of I_B
- that sets the values of V_{CE} and I_C

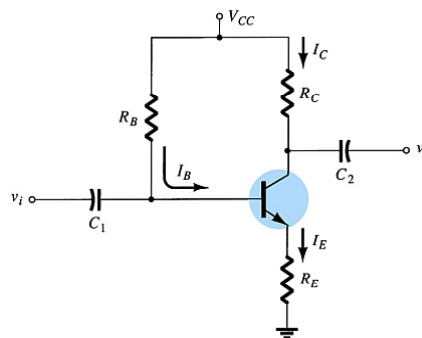2. Emitter-Stabilized Bias Circuit

Adding a resistor (R_E) to the emitter circuit stabilizes the bias circuit.



Base-Emitter Loop

From Kirchhoff's voltage law:


$$+V_{CC} - I_E R_E - V_{BE} - I_E R_E = 0$$

Since $I_E = (\beta + 1)I_B$:

$$V_{CC} - I_B R_B - (\beta + 1)I_B R_E = 0$$

Solving for I_B :
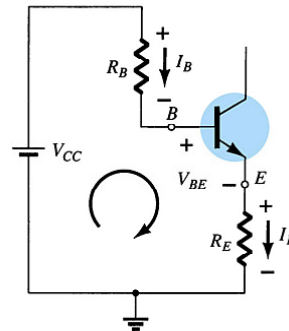
$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E}$$



Collector-Emitter Loop

From Kirchhoff's voltage law:

$$I_E R_E + V_{CE} + I_C R_C - V_{CC} = 0$$

Since $I_E \cong I_C$:


$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

Also:

$$V_E = I_E R_E$$

$$V_C = V_{CE} + V_E = V_{CC} - I_C R_C$$
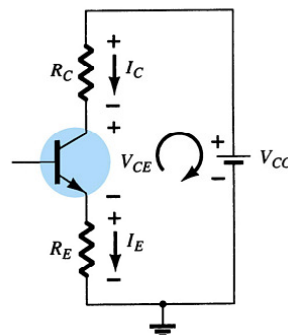
$$V_B = V_{CC} - I_B R_B = V_{BE} + V_E$$





Improved Biased Stability

Stability refers to a circuit condition in which the currents and voltages will remain fairly constant over a wide range of temperatures and transistor Beta (β) values.

Adding R_E to the emitter improves the stability of a transistor.

Saturation Level

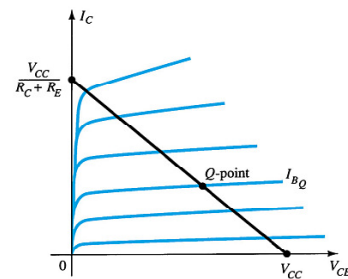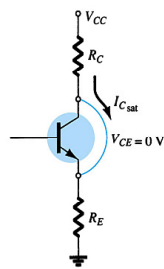

The endpoints can be determined from the load line.

$V_{CEcutoff}$:

$$\begin{aligned} V_{CE} &= V_{CC} \\ I_C &= 0 \text{ mA} \end{aligned}$$


I_{Csat} :

$$\begin{aligned} V_{CE} &= 0 \text{ V} \\ I_C &= \frac{V_{CC}}{R_C + R_E} \end{aligned}$$

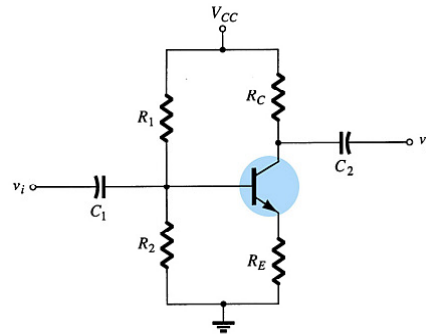3. Voltage Divider Bias

This is a very stable bias circuit.

The currents and voltages are nearly independent of any variations in β .



Approximate Analysis

Where $I_B \ll I_1$ and $I_1 \cong I_2$:

$$V_B = \frac{R_2 V_{CC}}{R_1 + R_2}$$

Where $\beta R_E > 10 R_2$:

$$I_E = \frac{V_E}{R_E}$$


$$V_E = V_B - V_{BE}$$

From Kirchhoff's voltage law:

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

$$I_E \cong I_C$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

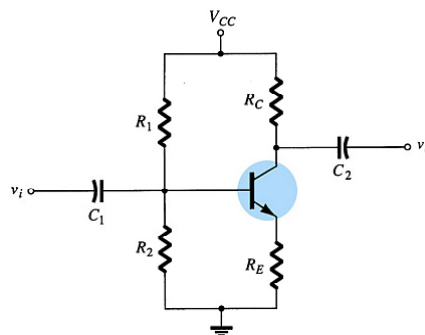

Voltage Divider Bias Analysis

Transistor Saturation Level

$$I_{C\text{sat}} = I_{C\text{max}} = \frac{V_{CC}}{R_C + R_E}$$

Load Line Analysis

Cutoff:

$$V_{CE} = V_{CC}$$

$$I_C = 0\text{mA}$$


Saturation:

$$I_C = \frac{V_{CC}}{R_C + R_E}$$

$$V_{CE} = 0\text{V}$$

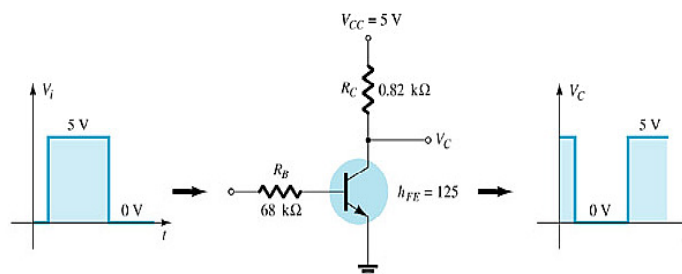4. Transistor Switching Networks

Transistors with only the DC source applied can be used as electronic switches.



Switching Circuit Calculations

Saturation current:

$$I_{Csat} = \frac{V_{CC}}{R_C}$$


To ensure saturation:

$$I_B > \frac{I_{Csat}}{\beta_{dc}}$$

Emitter-collector resistance at saturation and cutoff:

$$R_{sat} = \frac{V_{CEsat}}{I_{Csat}}$$

$$R_{cutoff} = \frac{V_{CC}}{I_{CEO}}$$

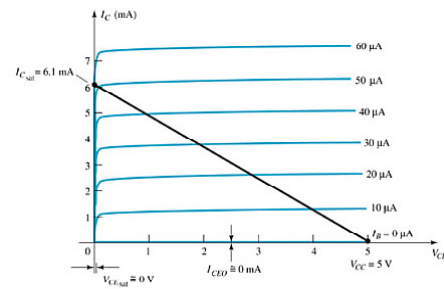


Switching Time

Transistor switching times:

$$t_{on} = t_r + t_d$$

$$t_{off} = t_s + t_f$$

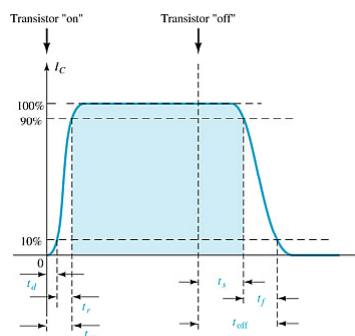

Troubleshooting Hints

- Approximate voltages
 - $V_{BE} \cong .7 \text{ V}$ for silicon transistors
 - $V_{CE} \cong 25\% \text{ to } 75\% \text{ of } V_{CC}$
- Test for opens and shorts with an ohmmeter.
- Test the solder joints.
- Test the transistor with a transistor tester or a curve tracer.
- Note that the load or the next stage affects the transistor operation.

PNP Transistors

The analysis for *pnp* transistor biasing circuits is the same as that for *nnp* transistor circuits. The only difference is that the currents are flowing in the opposite direction.