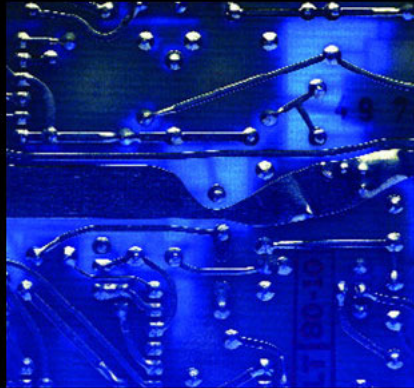


ELECTRONIC DEVICES AND CIRCUIT THEORY

TENTH EDITION

BOYLESTAD



PEARSON

Chapter 3: Bipolar Junction Transistors



Transistor Construction

There are two types of transistors:

- *pn**p*
- *np**n*

The terminals are labeled:


- **E** - Emitter
- **B** - Base
- **C** - Collector

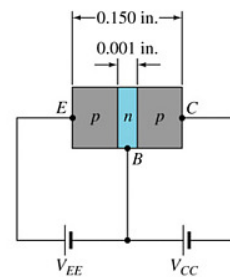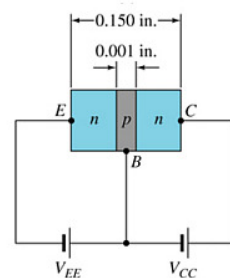*pn**p**np**n*

Transistor Operation

With the external sources, V_{EE} and V_{CC} , connected as shown:

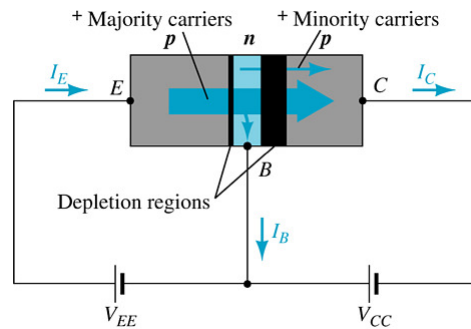- The emitter-base junction is forward biased
- The base-collector junction is reverse biased



3


Currents in a Transistor

Emitter current is the sum of the collector and base currents:

$$I_E = I_C + I_B$$


The collector current is comprised of two currents:
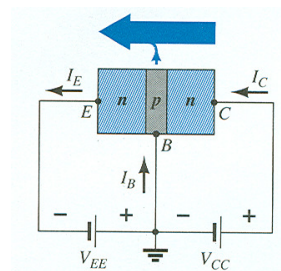
$$I_C = I_{C_{\text{majority}}} + I_{C_{\text{minority}}}$$




4

Common-Base Configuration

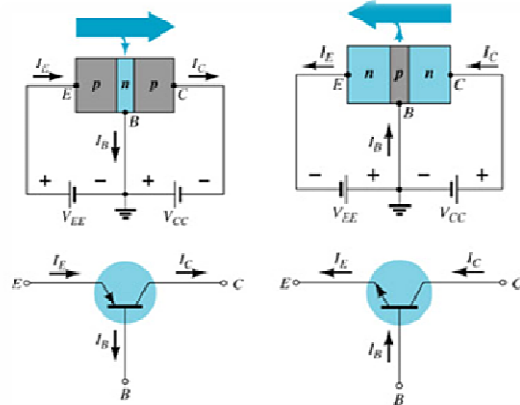


The base is common to both input (emitter–base) and output (collector–base) of the transistor.

5

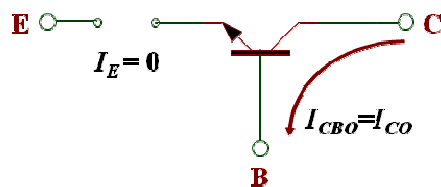

Reverse saturation current

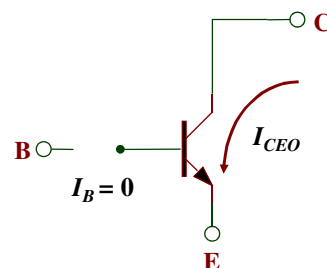


Circuit conditions related to I_{CEO} .

Common-Base Amplifier

Input Characteristics

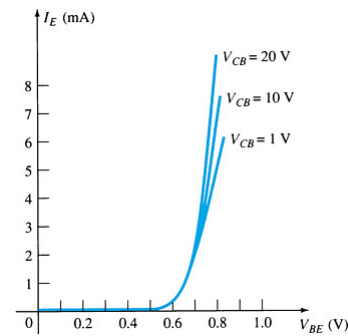This curve shows the relationship between of input current (I_E) to input voltage (V_{BE}) for three output voltage (V_{CB}) levels.




7

Common-Base Amplifier

Output Characteristics

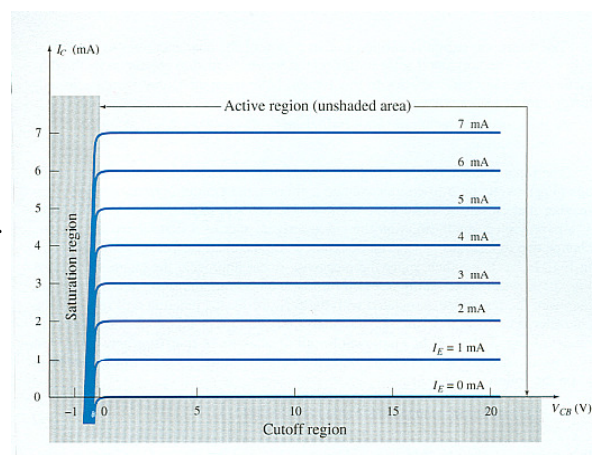This graph demonstrates the output current (I_C) to an output voltage (V_{CB}) for various levels of input current (I_E).



8

Operating Regions

- **Active** – Operating range of the amplifier. *In the active-region the base-emitter junction is forward-biased, whereas the collector-base junction is reverse-biased.*
- **Cutoff** – The amplifier is basically off. There is voltage, but little current. *In the cutoff region the base-emitter and collector-base junctions of a transistor are both reverse-biased.*
- **Saturation** – The amplifier is full on. There is current, but little voltage. *In the saturation region the base-emitter and collector-base junctions are forward-biased.*

9

Approximations

Emitter and collector currents:

$$I_C \cong I_E \quad (\text{in the active region})$$

Base-emitter voltage:

$$V_{BE} = 0.7 \text{ V (for Silicon) (also transistor "on" state voltage)}$$

Alpha (α)

Alpha (α) is the ratio of I_C to I_E :

$$\alpha_{dc} = \frac{I_C}{I_E}$$

Ideally: $\alpha = 1$


In reality: α is between 0.9 and 0.998

10

Common-Emitter Configuration


The emitter is common to both input (base-emitter) and output (collector-emitter).

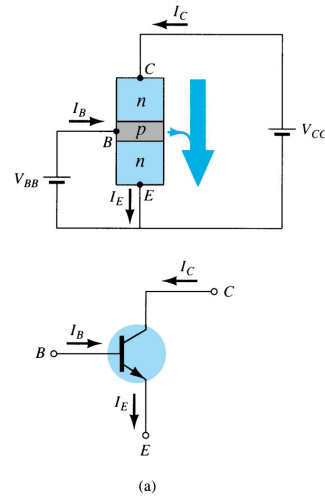The input is on the base and the output is on the collector.




11

Common-Emitter Characteristics

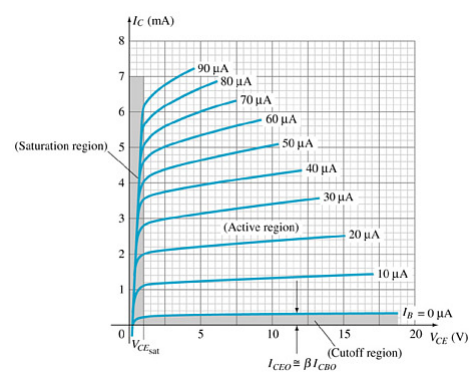

Collector Characteristics

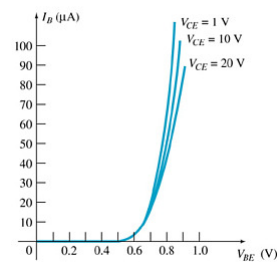

Base Characteristics

12

Operating Regions

- **Active** – Operating range of the amplifier. *In the active-region of a common-emitter amplifier, the base-emitter junction is forward-biased, whereas the collector-base junction is reverse-biased.*
- **Cutoff** – The cutoff region for the common-emitter configuration is not well defined as for the common-base configuration. Note on the collector characteristics of the figure on the previous slide that I_C is not equal to zero when I_B is zero. *For linear amplification purposes, cutoff for the common-emitter configuration will be defined by $I_C = I_{CEO}$.*
- When employed as a switch in the logic circuitry, a transistor will have two points of operation of interest: one in the cutoff and one in the saturation region. The cutoff condition should ideally be $I_C = 0\text{mA}$ for the chosen V_{CE} voltage. Since I_{CEO} is typically low in magnitude for silicon materials, *cutoff will exist for switching purposes when $I_B = 0\mu\text{A}$ or $I_C = I_{CEO}$ for silicon transistors only. For germanium transistors, however, cutoff for switching purposes will be defined as those conditions that exist when $I_C = I_{CBO}$.* This condition can be obtained for germanium transistors by reverse-biasing the base-to-emitter junction a few tenths of a volt.

13

Common-Emitter Amplifier Currents

Ideal Currents

$$I_E = I_C + I_B \qquad I_C = \alpha I_E$$

Actual Currents

$$I_C = \alpha I_E + I_{CBO} \quad \text{where } I_{CBO} = \text{minority collector current}$$

I_{CBO} is usually so small that it can be ignored, except in high power transistors and in high temperature environments.

When $I_B = 0\mu\text{A}$ the transistor is in **cutoff**, but there is some minority current flowing called I_{CEO} .

$$I_{CEO} = \frac{I_{CBO}}{1 - \alpha} \Big|_{I_B = 0\mu\text{A}}$$

14

Beta (β)

β represents the amplification factor of a transistor. (β is sometimes referred to as h_{fe} , a term used in transistor modeling calculations)

In DC mode:

$$\beta_{dc} = \frac{I_C}{I_B}$$

Relationship between amplification factors β and α

$$\alpha = \frac{\beta}{\beta + 1} \quad \beta = \frac{\alpha}{\alpha - 1}$$


Relationship Between Currents

$$I_C = \beta I_B \quad I_E = (\beta + 1) I_B$$

15

Common-Collector Configuration

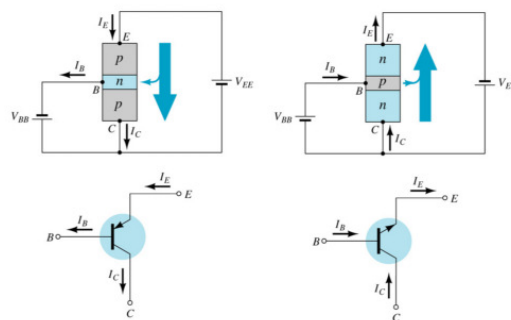
The input is on the base and the output is on the emitter.



16

Common–Collector Configuration

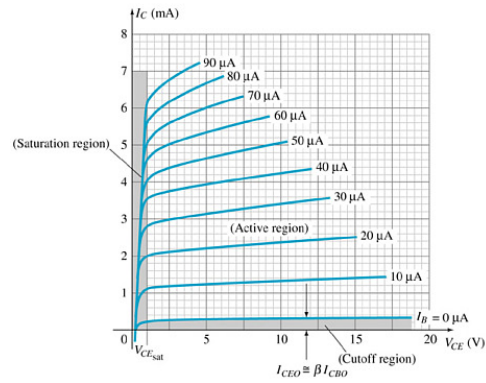The characteristics are similar to those of the common-emitter configuration, except the vertical axis is I_E .




17

Operating Limits for Each Configuration

The *cutoff* region is defined as that region below $I_C = I_{CEO}$. V_{CE} is at maximum and I_C is at minimum ($I_{Cmax} = I_{CEO}$) in the **cutoff region**.

I_C is at maximum and V_{CE} is at minimum ($V_{CEmax} = V_{CEsat} = V_{CEO}$) in the **saturation region**.

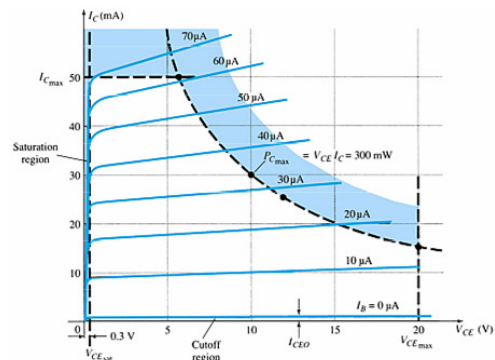
The transistor operates in the **active region** between saturation and cutoff.



18


Transistor Testing

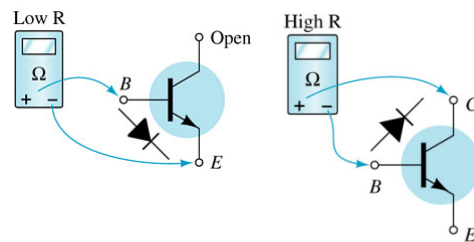- **Curve Tracer**
Provides a graph of the characteristic curves.
- **DMM**
Some DMMs measure β_{DC} or h_{FE} .
- **Ohmmeter**



19

Transistor Terminal Identification

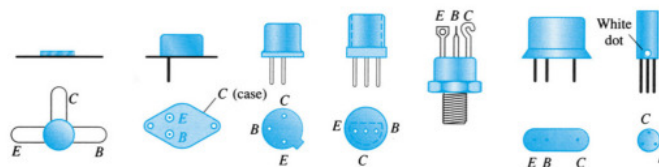

20